
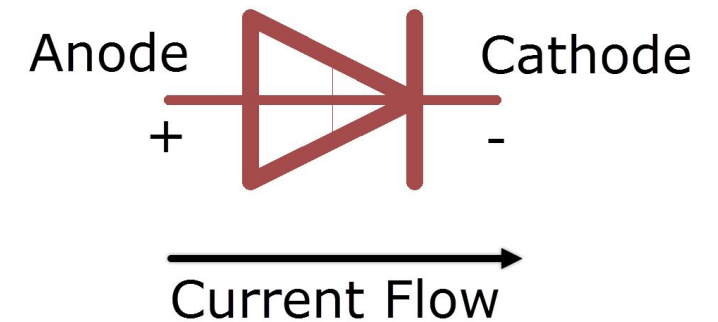


HyTech Racing Charging Circuits Training


2019-2020

- If you would like to officially join HyTech Racing, you can pay dues using **Venmo**, **PayPal**, **Square**, or **Cash**.
 - Venmo: **@hytechracing**
 - PayPal: **gthytech@gmail.com**
 - Square: **<https://squareup.com/store/hytech-racing>**
 - Cash: **See an Officer**
- Paying dues gets you access to our Slack, Trello, Github, and Google Drive.
- Deadline is 9/15.

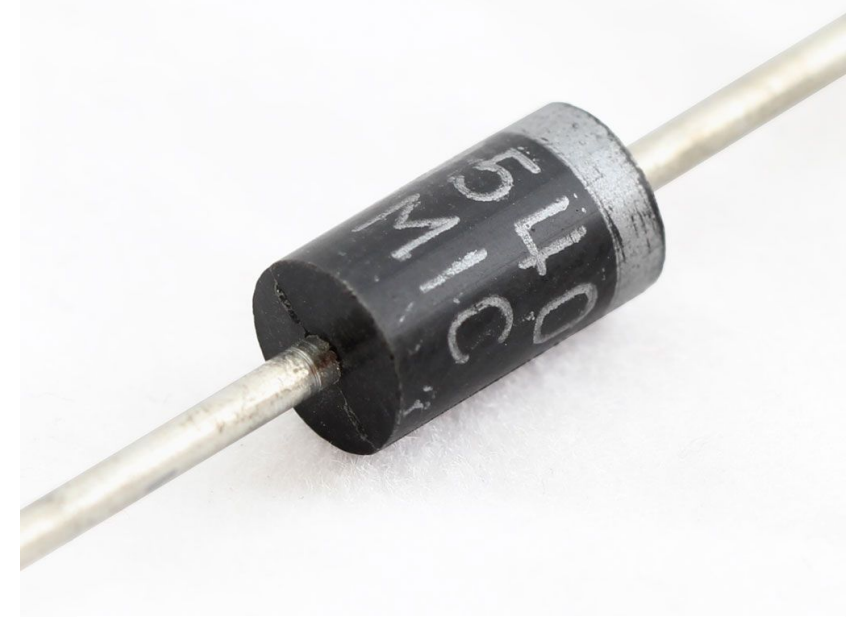
- A **diode** is a two-terminal device that conducts current primarily in **one direction**:
 - It has a very **low resistance** in one direction after a certain voltage.
 - It has a very **high resistance** in another direction.
- There are several different kinds of common diodes:
 - **LEDs** emit light.
 - **PN Junction diodes** are the main diodes HyTech uses.



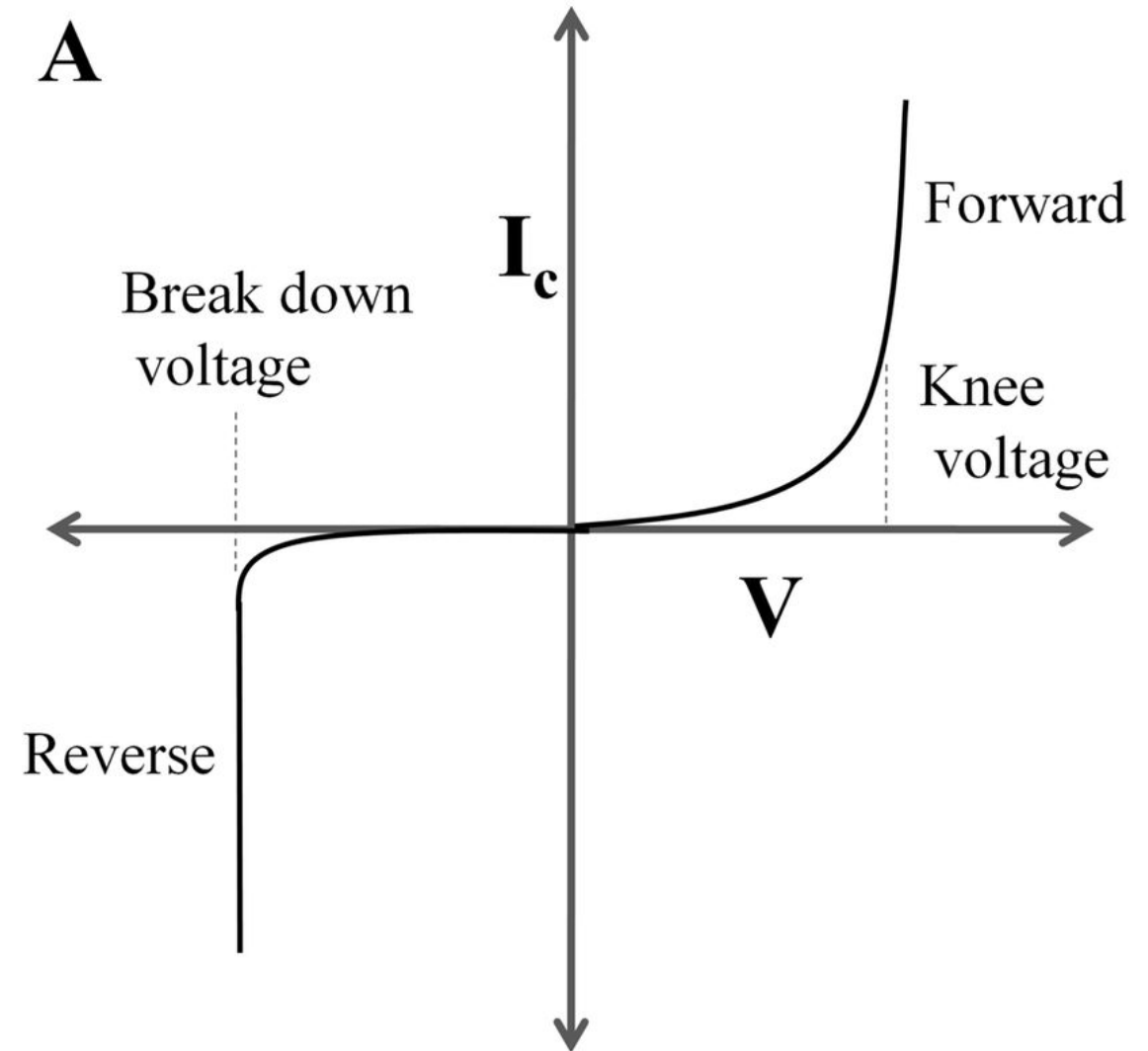- Diodes have a **bias** or direction.
- Diodes have a **knee voltage**.
 - Before its knee voltage, the diode has a very high resistance.
 - After the knee voltage, the diode has a very low resistance.
- Diodes have a **breakdown voltage** or **reverse bias voltage**.
 - This is the maximum voltage that can be applied in reverse.
 - Beyond this point usually causes **damage** to the diode.




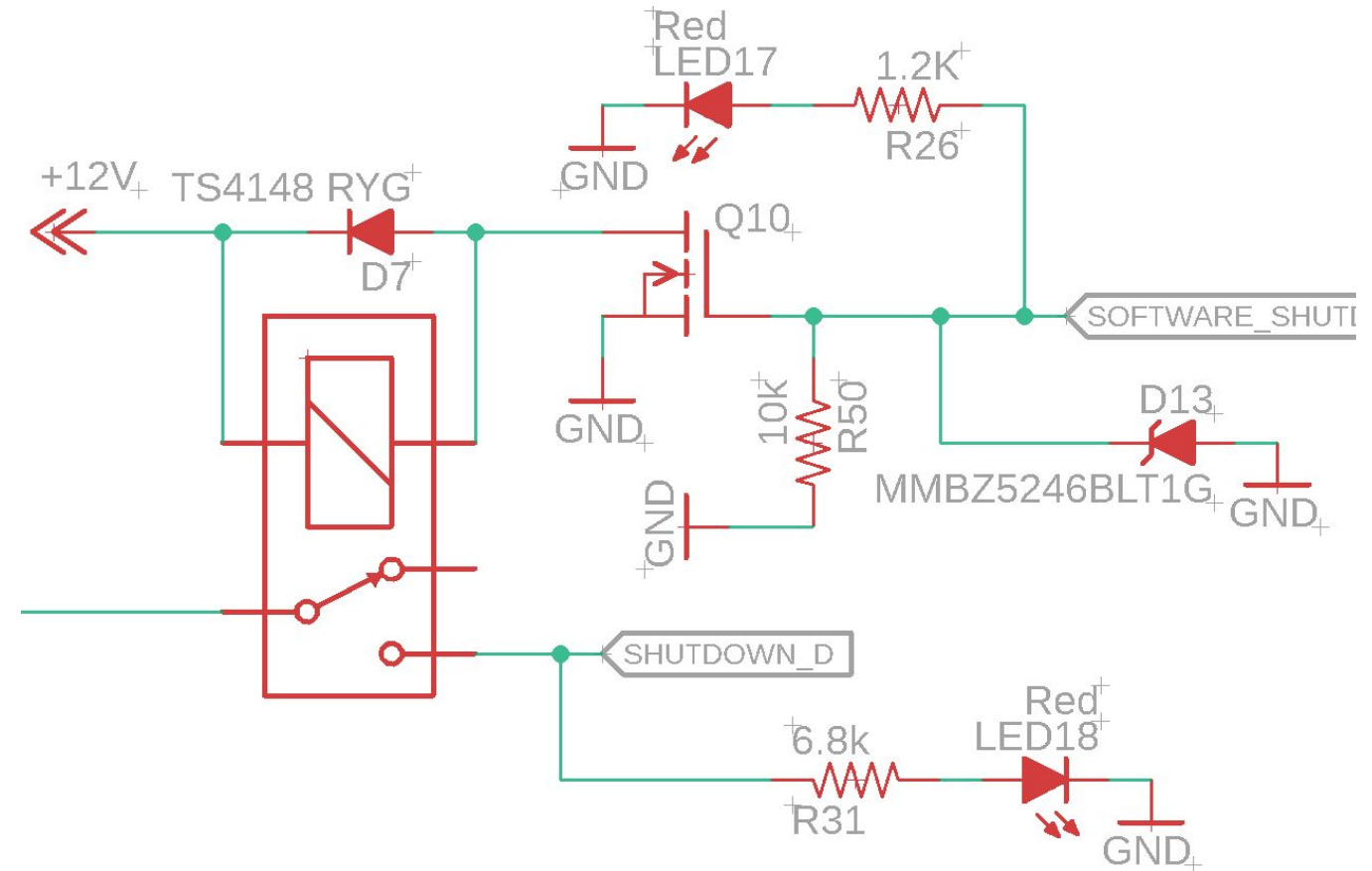- A **flyback diode** (**D7** in the schematic) is a PN Junction diode used to eliminate voltage spikes.
 - The reason for those spikes is complicated, but is due to the change in state of the big square relay.
- LEDs (**LED17** and **LED18** in the schematic) are used as status indications.
 - These are especially useful in debugging.




Light Emitting Diodes (LEDs)

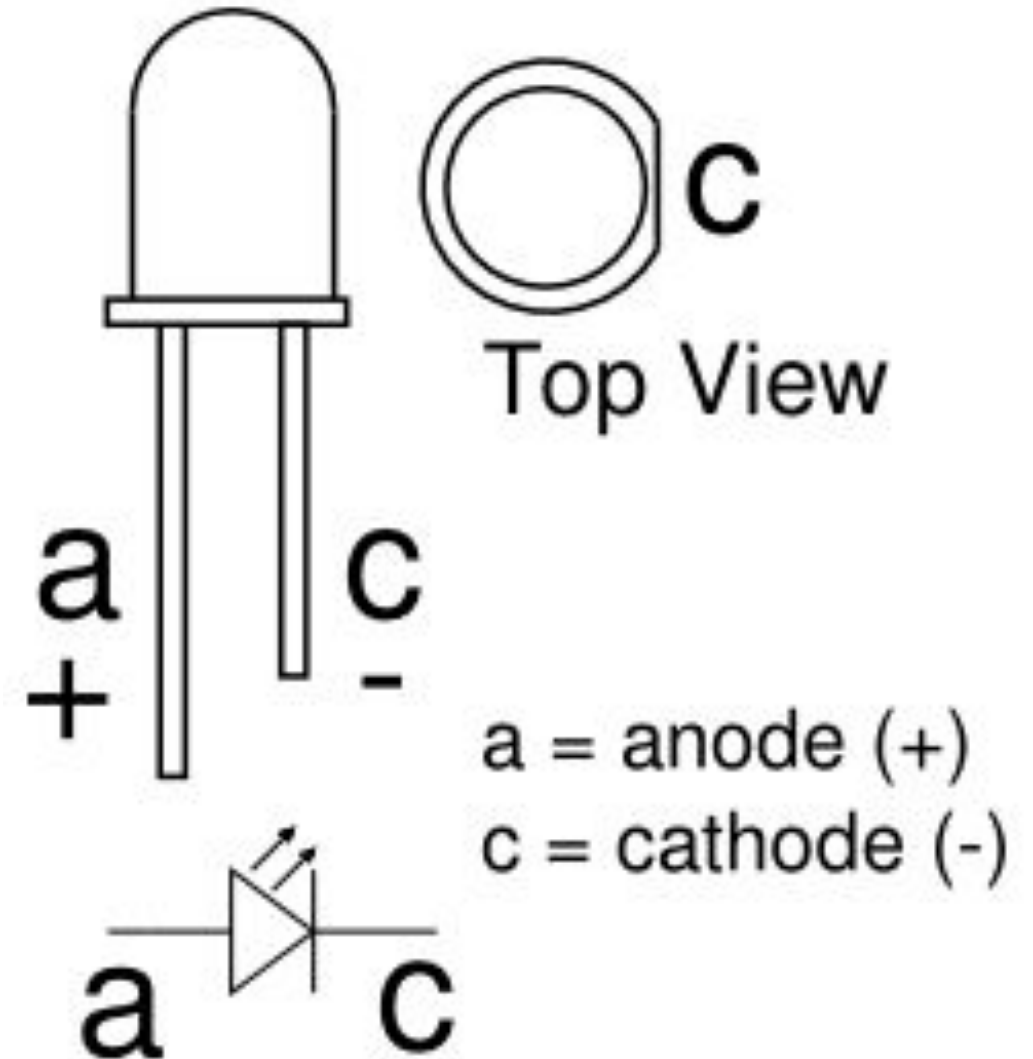- A **LED** is a two-terminal **diode** that **emits light** when current passes through it.
- It acts like a normal diode otherwise.
- It is important, however, to maintain a constant current for a steady brightness.
 - That value is usually listed in a datasheet.
 - Every color of LEDs have a different relationship between voltage and resistor.





- The goal is to send a **constant current** to the LED.
- That means, if we have a known input voltage into the circuit, we need to figure out what resistor we need in series with the LED.
- It requires use of a **Current vs. Voltage Curves** like the one the right.
- If there is a 5V input, and 20mA needs to go through the LED:
 - We need to have 3.5V through the LED and 1.5V through the resistor ($5V - 3.5V = 1.5V$) and now apply Ohm's Law.
 - It should be a 75Ω resistor from $1.5V / 20mA = 75\Omega$.


Forward Current vs. Forward Voltage

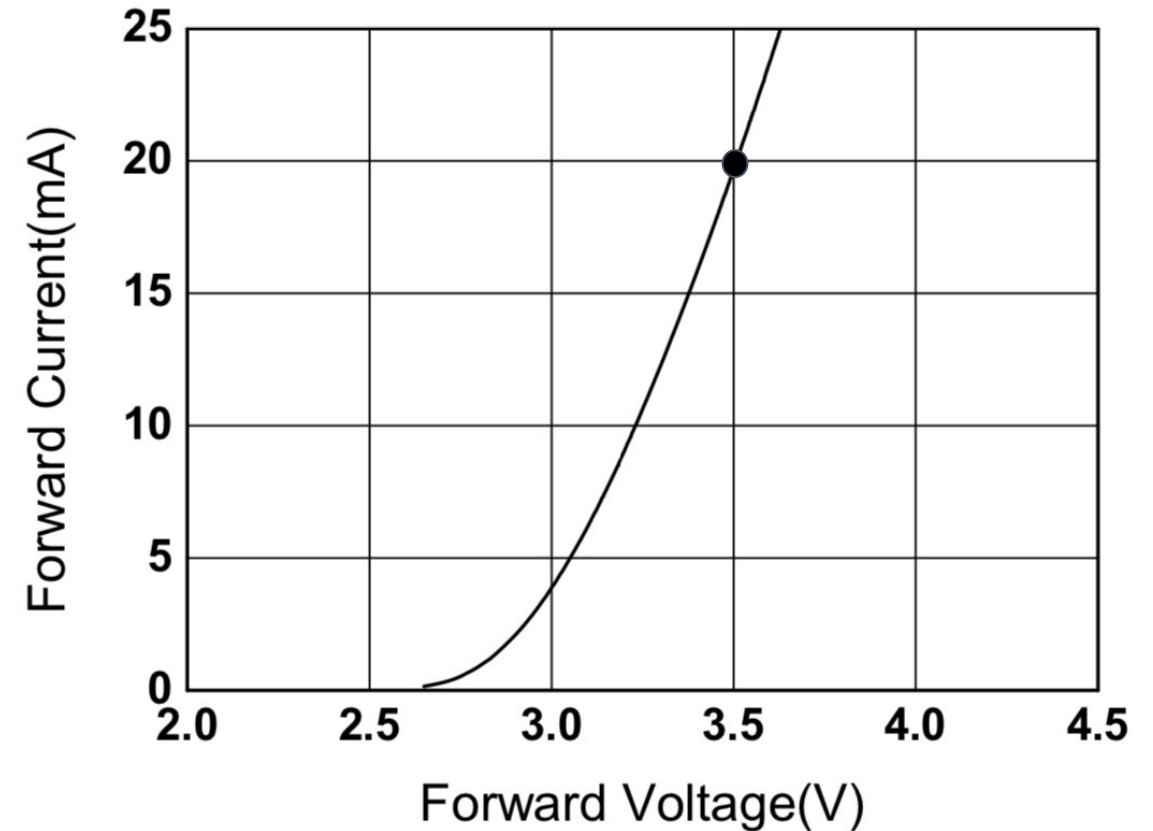

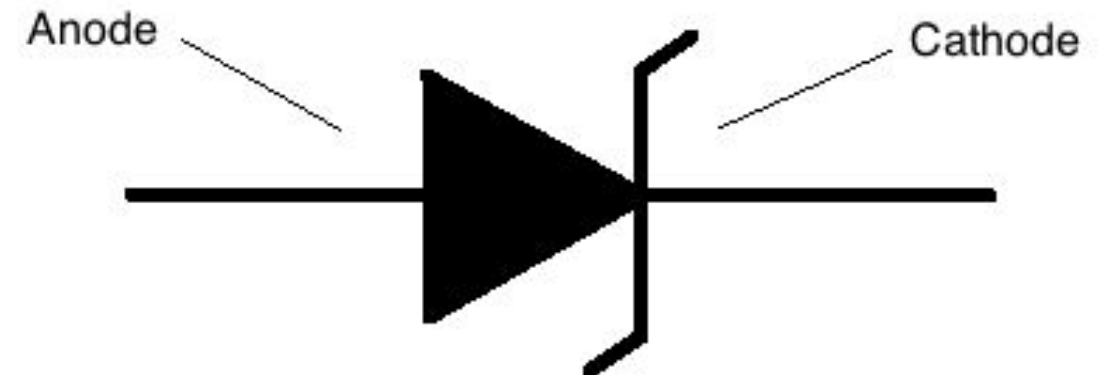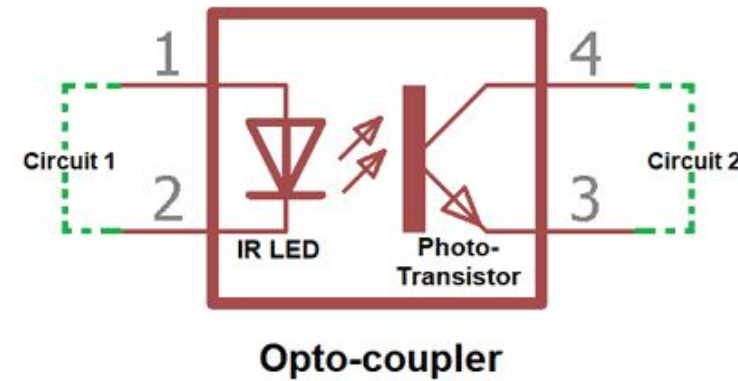- **Optocouplers** are a special integrated circuit that uses LEDs to **switch other components on and off**.
- **Zener diodes** are used to suppress voltage spikes and to **regulate voltage**.
 - **Transient Voltage Suppression (TVS) diodes** are made up of multiple zener diodes and provide specialized **bi-directional voltage spike suppression**.






- Zener diodes have **two knee voltages**.
- Between the two, and for positive voltages above the knees, zeners act like **normal diodes**.
- At the zener diode's **reverse voltage** however, it begins to conduct again.
 - It **does not breakdown** like normal diodes do.
- This allows us to **clamp** or **suppress** voltages above this point.
 - This means we lock the range of voltages we can have to eliminate sudden spikes in voltages or **transient voltages** which could destroy components in our circuit


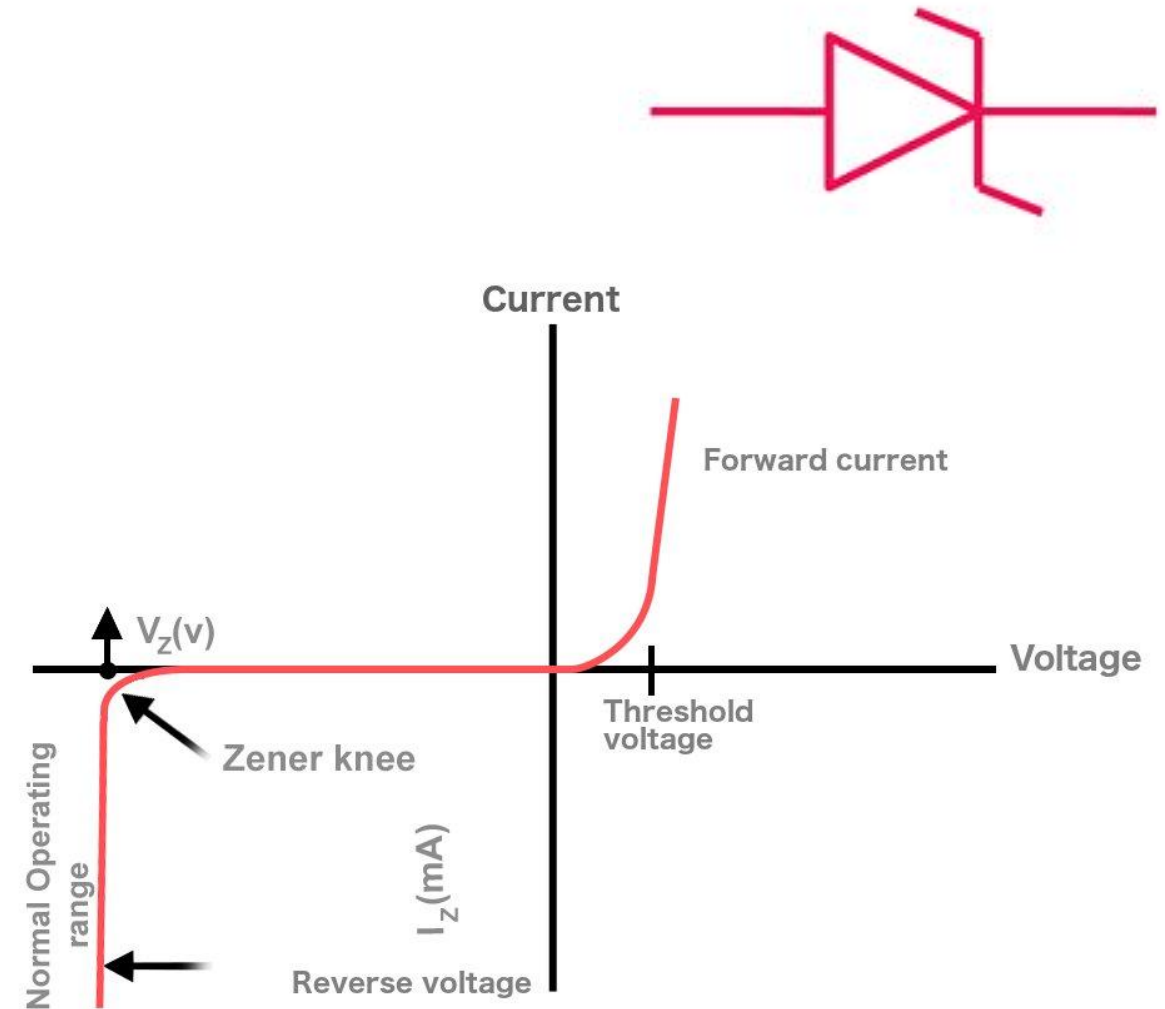


Voltage Suppression

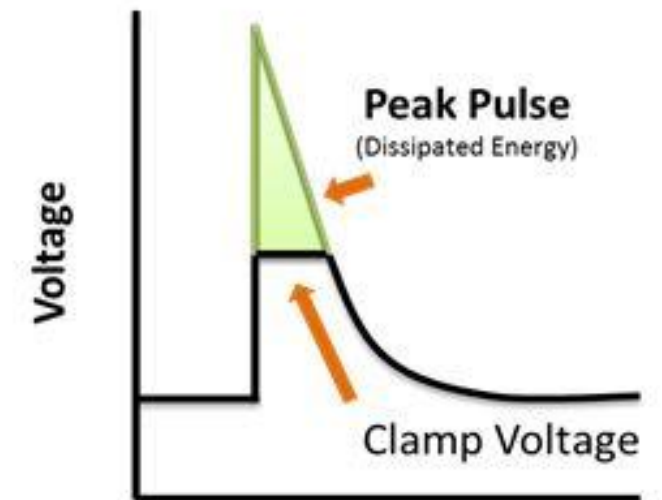
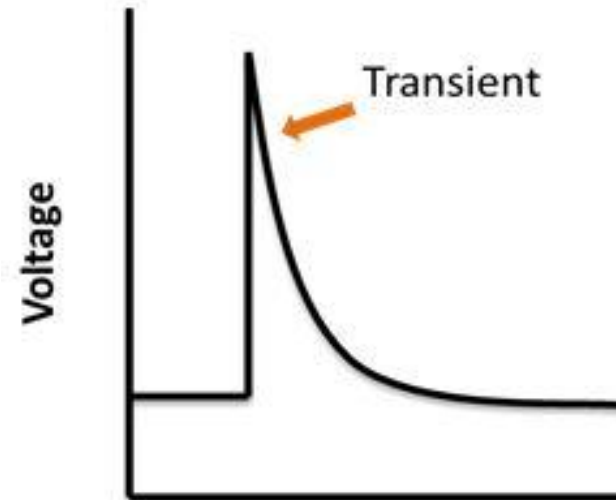
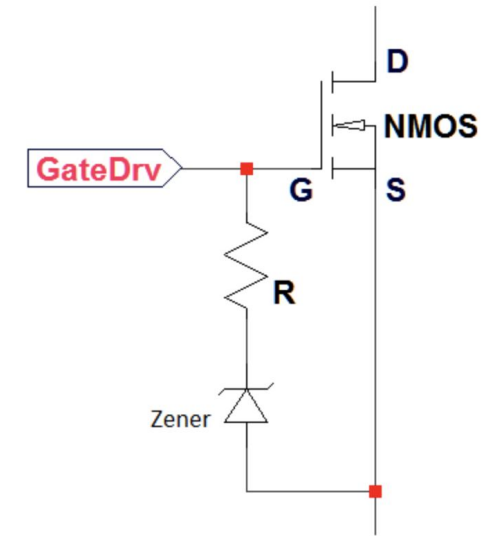
- We already discussed MOSFETs as a type of transistor.
 - The pin that turns them on or off is called the **gate**.
 - That pin is very **vulnerable to damage** from transient voltages.
- Placing a zener diode between the **gate** and **ground** limits these spikes to the zener's reverse voltage, protecting the mosfet




- A TVS diode is made up of **two zener diodes in opposition**.
 - A single zener conducts when its voltage is outside of the range of its bias voltages (commonly **-15V** and **0.7V**).
 - Combining two zeners lets you set a positive and lower bound (**-15V** to **15V**).
- A TVS diode thus **limits the potential difference** between two points in the circuit.
 - This property makes them useful for protecting **differential signals**.

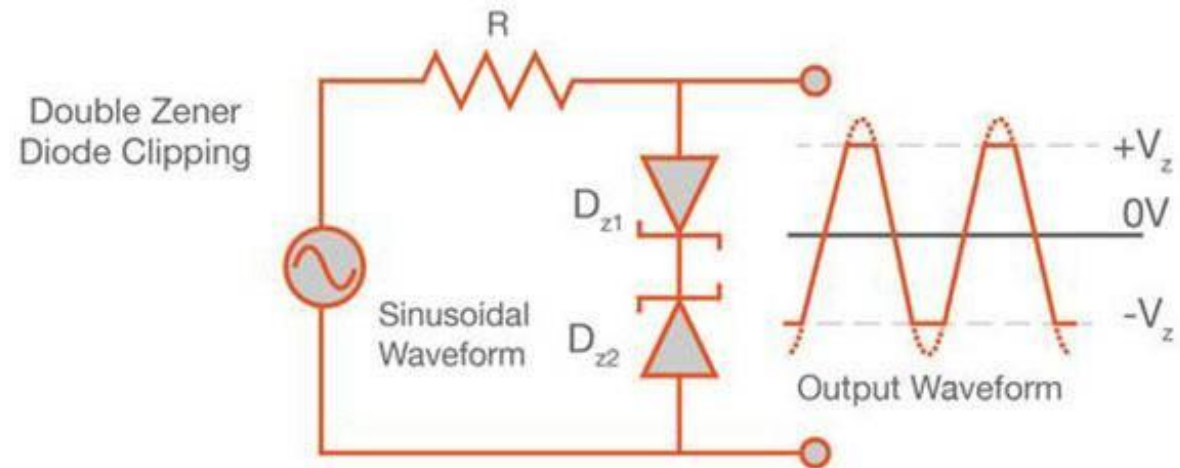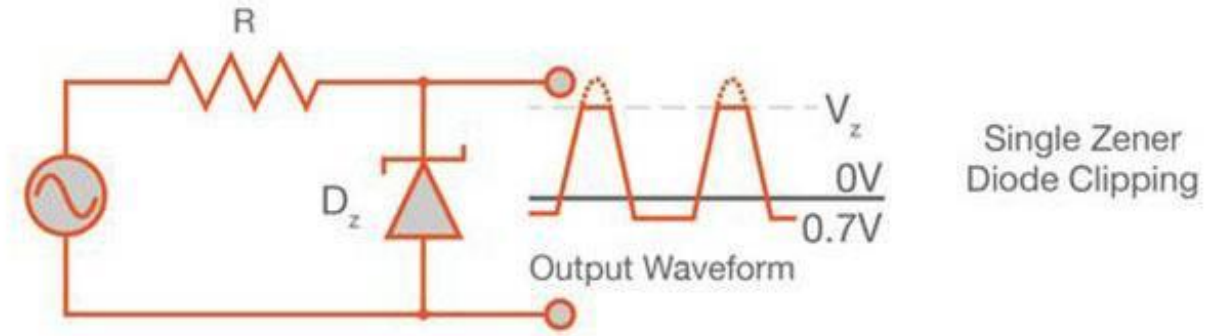

- A **relay** is device used to switch another part of a circuit on or off while remaining **isolated**.
- Similar to diodes, there are several types:
 - **Mechanical relays** use a **magnetic coil** to physically switch a contact and are used in our shutdown circuit.
 - **Solid state relays** are another name for a **optocoupler**, using a LED to switch states.
- For each type, there are two versions:
 - **Normally open**
 - **Normally closed**

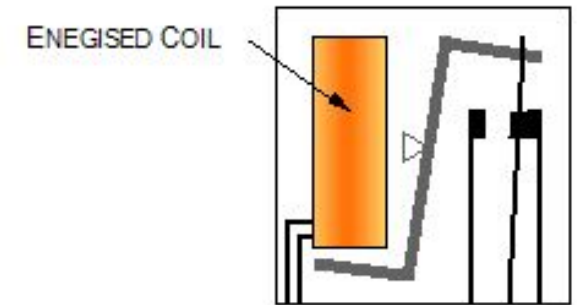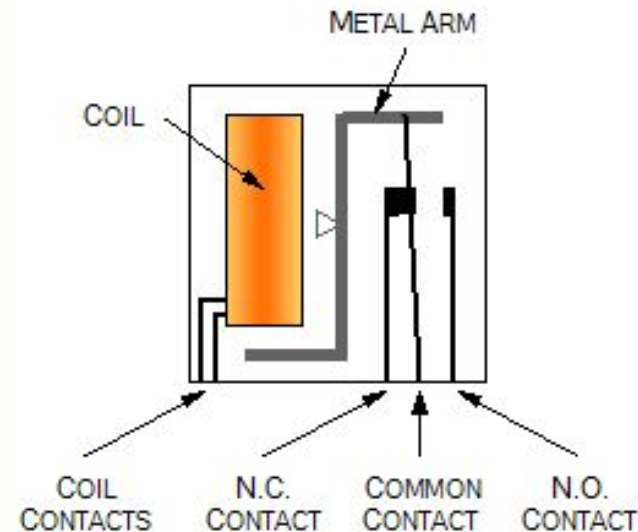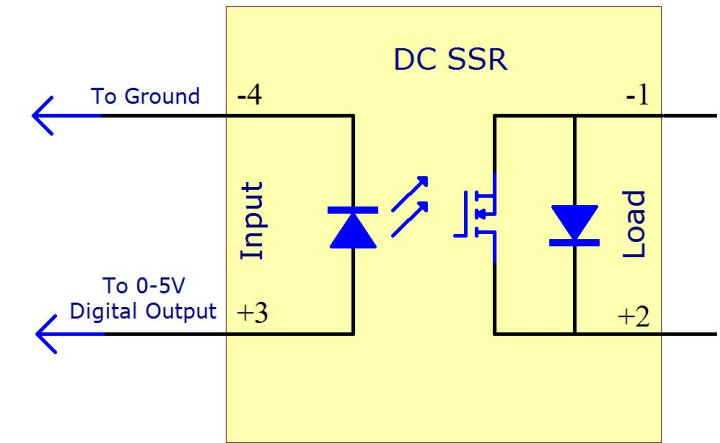


- A **relay (TS4148 RYG)** in the schematic) here is used for the shutdown circuit.
 - The line through it is labelled Shutdown_D
 - This is a normally open mechanical relay, so power through the coil **closes** the circuit, **enabling** the tractive system.
- There is a catch, mechanical relays are an **inductive load**.
 - That means they work best with a **constant current**.
 - Changing their state produces a **voltage spike** that can be up to **60V**, well more than the **5V** the rest of the circuit expects.

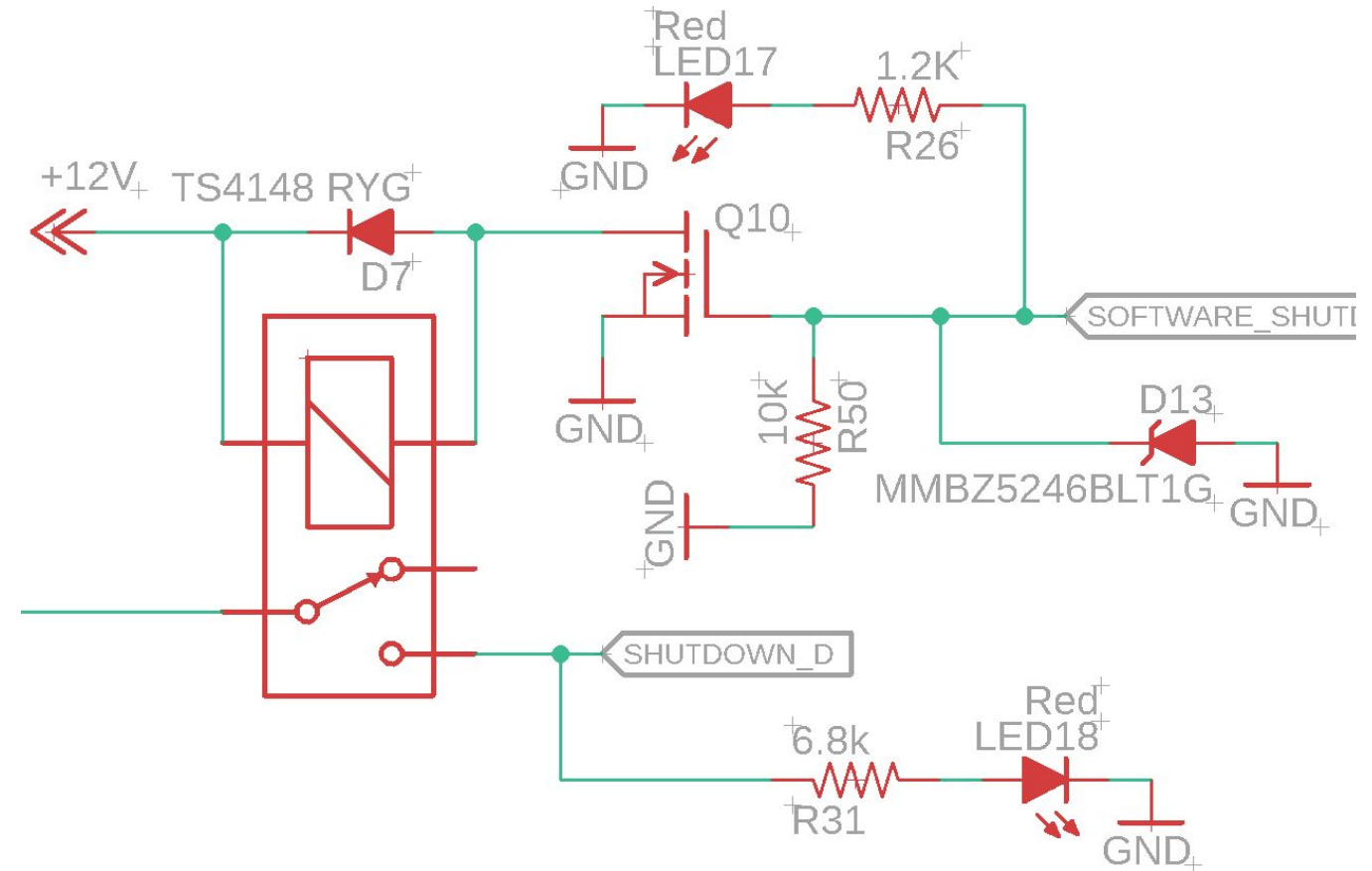


Control Area Network (CAN) Bus


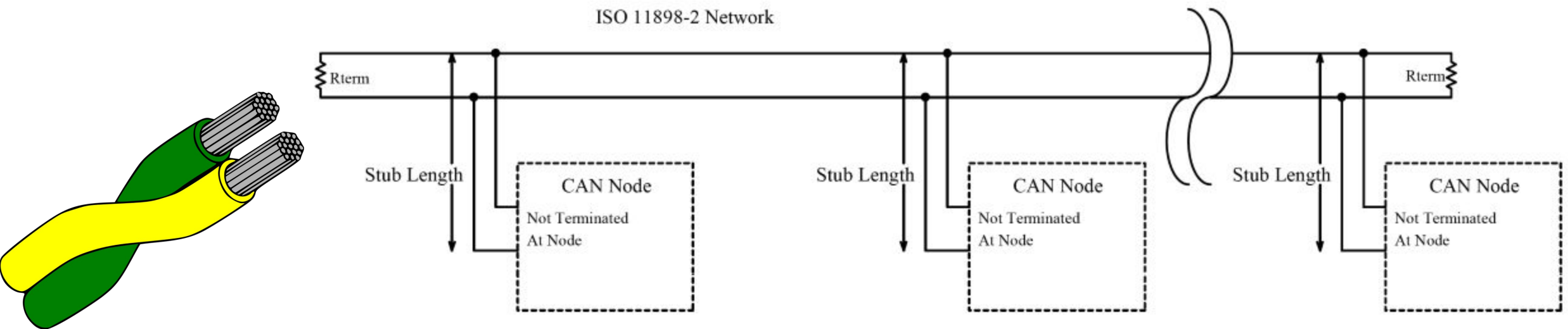
- The **Controller Area Network Bus** is the primary way devices in our car **communicate**.
 - It's an industry standard practice for automobiles.
- It uses **differential signaling** with **twisted pair wiring**, with one line being **CAN High (Yellow)** and **CAN Low (Green)**.
- It also has concepts of **nodes** and **data frames**.
- We use a **bus** topology.






CAN Bus Signaling

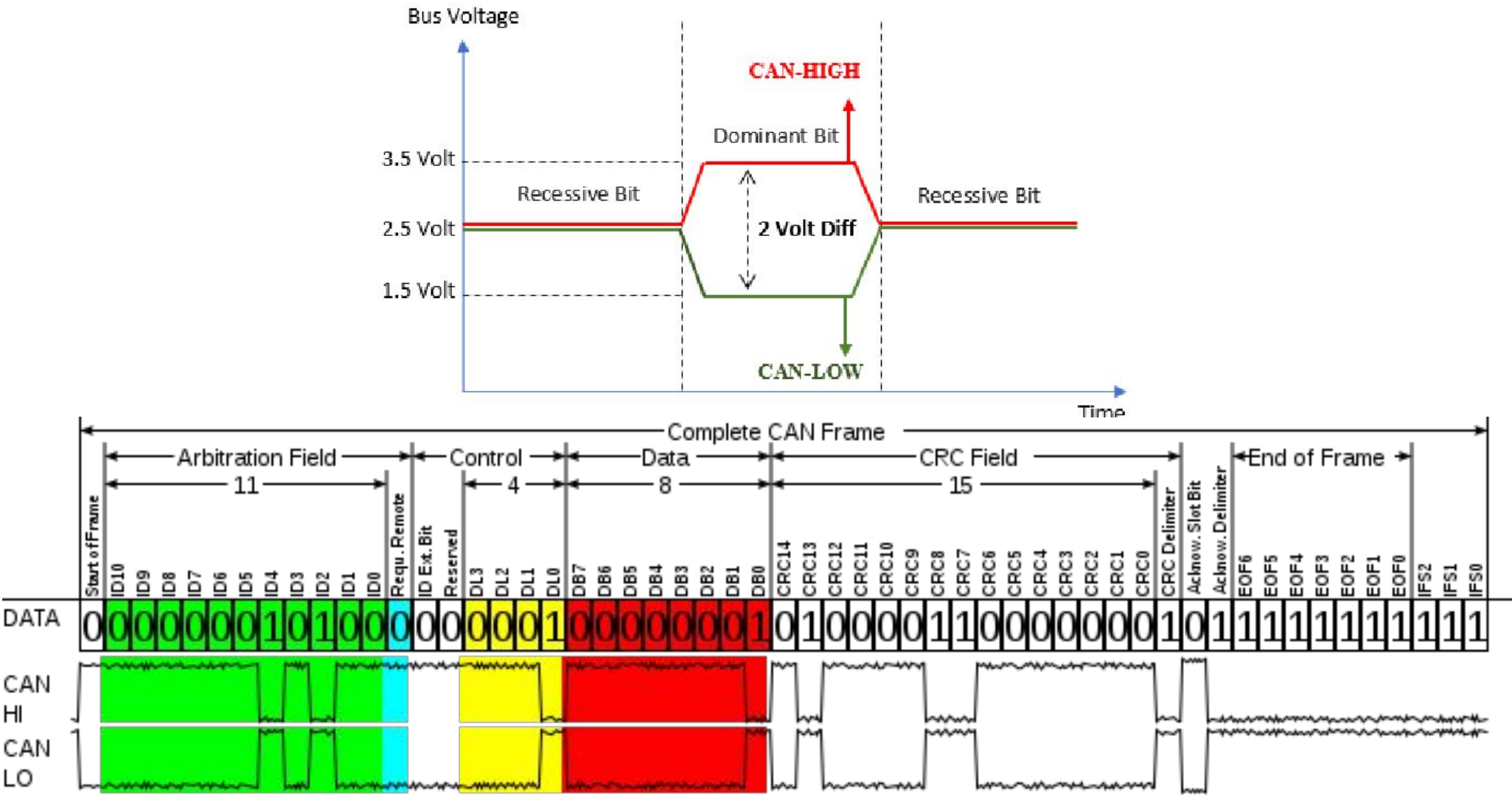

- The hardware for CAN is made up of a **controller** and a **transceiver**:
 - The transceiver converts **controller output** into **physical output** on the CAN lines and converts **physical input** to **controller input**.
 - The controller **packages the data** from the **microcontroller** to send to the transceiver and **packages transceiver data** to send to the **microcontroller**.
- We use the **MCP2551 Transceiver** and **MCP2515 Controller**.

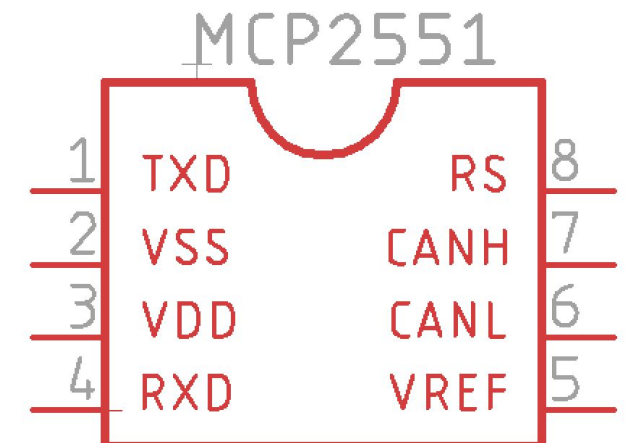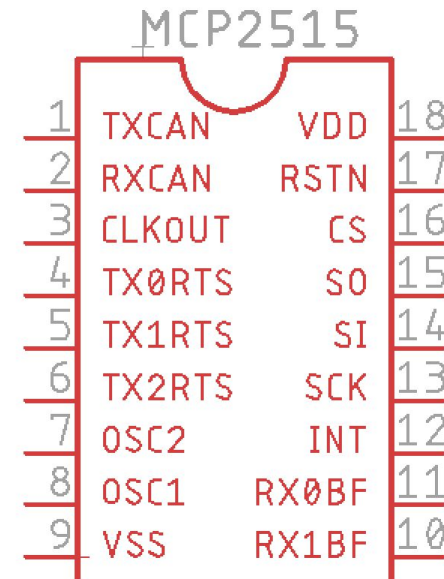

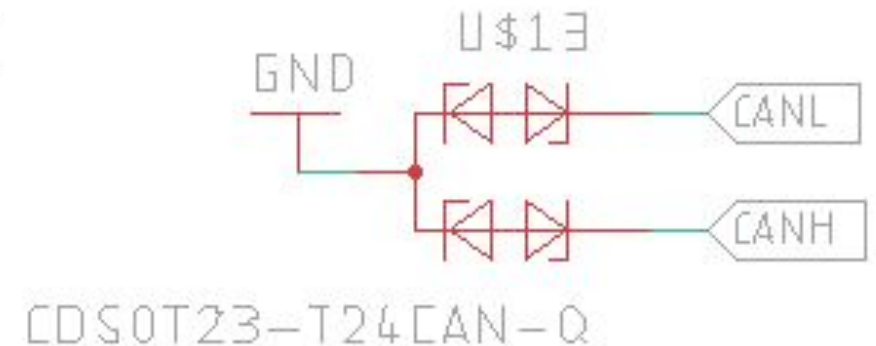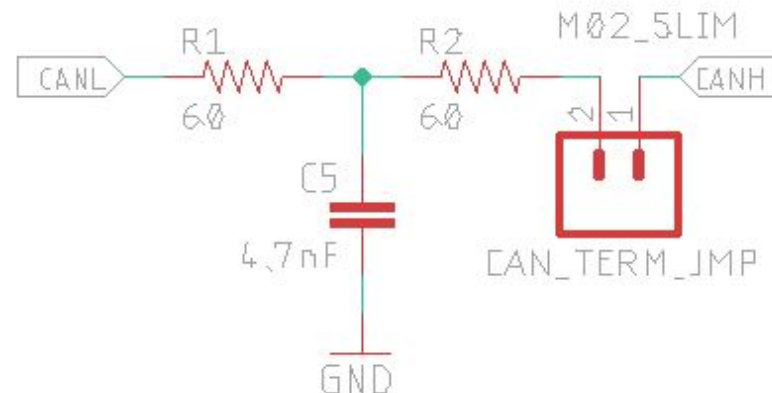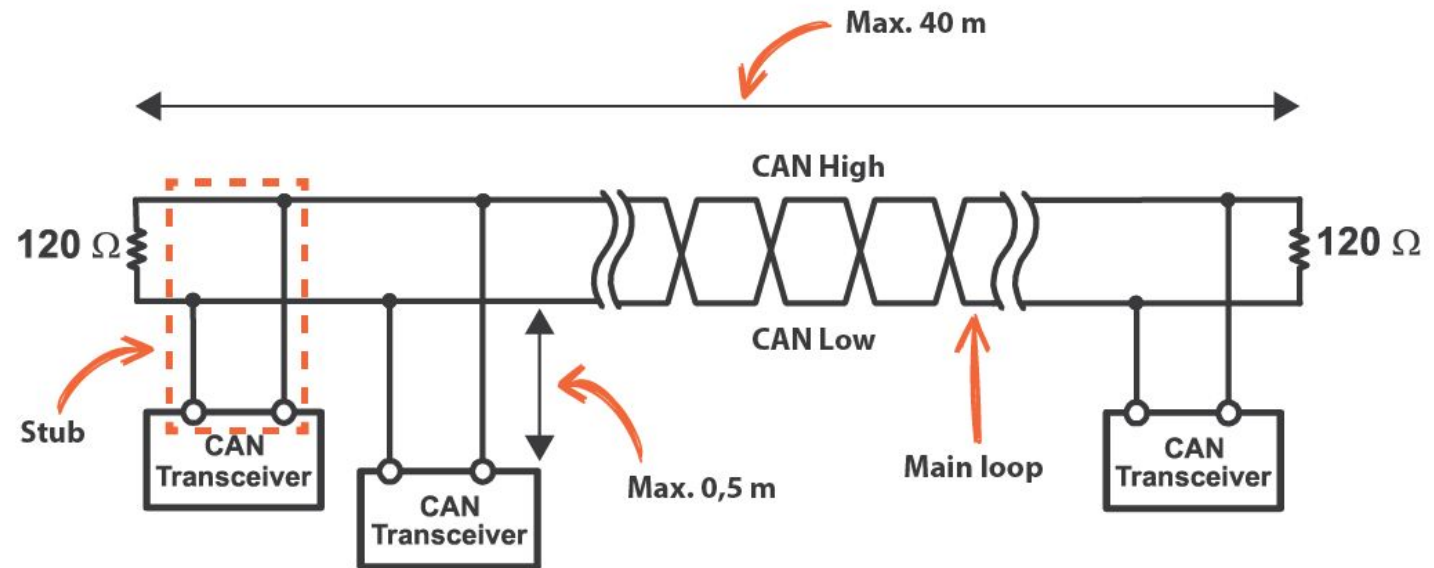- CAN requires **120 ohm termination resistors**
 - These resistors are necessary per specification to reduce **ringing**.
- We use **split termination** which uses a capacitor to further reduce noise between the signal lines.
- We use a pair of **TVS diodes** to protect the CAN lines from extreme voltages spikes.



Training Schedule

Date	Time	Location	Theme
Sunday 9/15	4:00pm - 6:00pm	SCC (Shop) AP Classroom	Safety